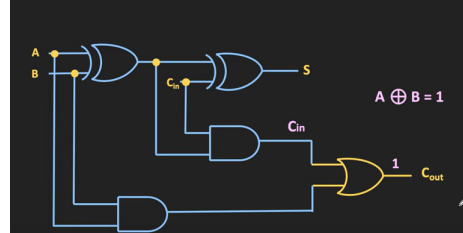


Carry Generation and Propagation



Relation	Unsigned Comparison	Signed Comparison
$A = B$	Z	Z
$A \neq B$	\bar{Z}	\bar{Z}
$A < B$	$C \cdot \bar{Z}$	$\bar{S} \cdot \bar{Z}$
$A > B$	\bar{C}	S
$A \leq B$	C	\bar{S}
$A \geq B$	$\bar{C} + Z$	$S + Z$

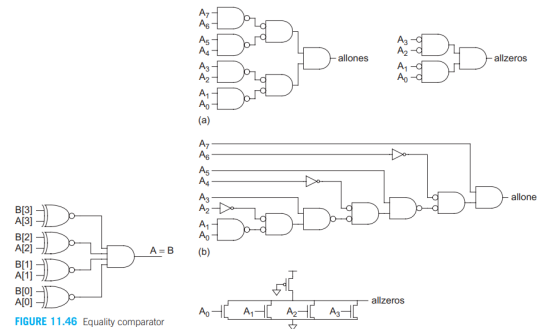


FIGURE 11.46 Equality comparator

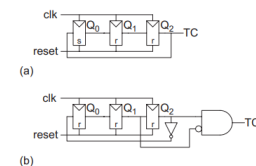


FIGURE 11.53 3-bit ring and Johnson counters

TABLE 11.6 Johnson counter sequence

Cycle	Q_0	Q_1	Q_2	TC
0	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	0	1	1	0
5	0	0	1	1
6	0	0	0	0

Repeats forever

Logical Shift:

- Shifts number left or right and fills with 0's
- 1011 LSR 1 = 0101 1011 LSL 1 = 0110

Arithmetic Shift:

- Shifts number left or right. Rt shift sign extends
- 1011 ASR 1 = 1101 1011 ASL 1 = 0110
- ASR of negative number remains negative (divide by power of 2)
- ASL = LSL (both stuff 0s in from the right/LSB side)

Rotate:

- Shifts number left or right and fills with lost bits
- 1011 ROR 1 = 1101 1011 ROL 1 = 0111

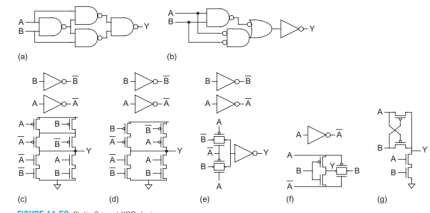


FIGURE 11.59 Static 2-input XOR designs

X marks the spot -- positions of XORs

p1, p2, p4, and p8 provide SEC; global parity p0 extends this to DED
Note positions and names of parity bits (always powers of 2 -- we'll see why)

Bit position	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
Encoded data bits	p1	p2	d1	p4	d2	d3	d4	p8	d5	d6	d7	d8	d9	d10	d11
Parity bit coverage	p1	p2	p4	p8											

p0 X X X X X X X X X X X X X X X X

9.24 NAND strategy Roll UP

9.24 Sketch a 3-input symmetric NAND gate. Show the currents as that the pull-up is four times as strong as the net worst-case pull-down. Label the transistor widths. Estimate the rising, falling, and average signal delays. How do they compare to a static CMOS 3-input NAND gate?

① $I_p = 4 I_N$ $\frac{W_u}{W_d} = 2$

② $I_p = I_N + I$ $I_p = \frac{4}{3} I_N + I$ $I_N = \frac{1}{3} I \Rightarrow \frac{W_u}{W_d} = \frac{4}{3}$

③ $I_p = \frac{4}{3} I$ $I_N = \frac{1}{3} I \Rightarrow \frac{W_u}{W_d} = \frac{4}{3}$

④ Roll down strength $\frac{1}{3} I + \frac{1}{3} I = \frac{2}{3} I$ $P = \frac{N}{\frac{4}{3} \cdot \frac{2}{3}}$

⑤ Roll up $\frac{1}{2} \cdot \frac{2}{3} - \frac{1}{3} = I$ $g_u = \frac{4}{3} \cdot \frac{1}{3} = 1$

9.21 Sketch a 3-input symmetric NOR gate. Show the currents so that the pull-up is four times as strong as the net worst-case pull-down. Label the transistor widths. Estimate the rising, falling, and average signal delays. How do they compare to a static CMOS 3-input NOR gate?

NOR is a stronger pull down


① $I_N = I_p + I$ $I_N = 4 I_p$ $\frac{W_u}{W_d} = 4$

② $I_N = I_p + I$ $I_N = 4 I_p$ $\frac{W_u}{W_d} = 4$

③ Pull up Current $I = 3 \cdot (\frac{1}{3} \cdot \frac{1}{3}) = \frac{1}{3}$ $g_{up} = \frac{10}{9}$

④ Pull down Current $I = \frac{4}{3} \cdot (\frac{1}{3} \cdot \frac{1}{3} + \frac{1}{3} \cdot \frac{1}{3}) = I$ $\frac{4}{3} \cdot \frac{1}{3} + \frac{1}{3} \cdot \frac{1}{3} = \frac{5}{9}$

standard xor/xnor circuit in CMOS

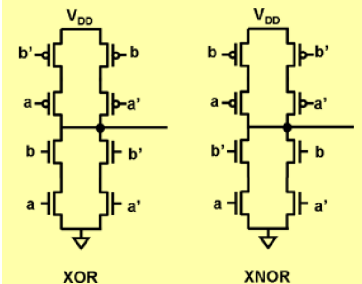

7.4

15,11

31,26

Transmitted Bits: 1 0 1 0 0 1 0

Received Bits: 1 1 1 0 0 1 0

C_3 C_2 C_1

C_1 3 5 7 and $P_1 = 0 \oplus 1 \oplus 1 = 0$

C_2 3 6 7 and $P_2 = 0 \oplus 1 \oplus 1 \oplus 1 = 1$

C_3 5 6 7 and $P_3 = 1 \oplus 1 \oplus 1 \oplus 0 = 1$

$C_3 C_2 C_1 = 6$

Extended Hamming Code: (Detect 2 errors and correct 1 error)

P D₄ D₃ D₂ P₃ D₁ P₂ P₁

8 7 6 5 4 3 2 1


Hamming Code for 7 bits: 1 0 1 0 0 1 0

Extended Hamming Code: 1 1 0 1 0 0 1 0 Even Parity


One Error: Received Bits: 1 1 1 0 0 1 0 Odd Parity $C_3 C_2 C_1$ not zero

Two Error: 1 1 1 0 0 1 0 Even Parity $C_3 C_2 C_1$ not zero

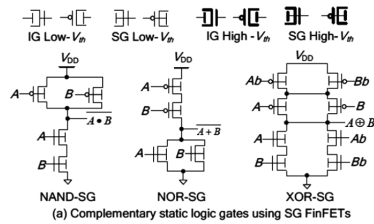
Error in P: 1 0 1 0 0 1 0 Odd Parity $C_3 C_2 C_1$ zero



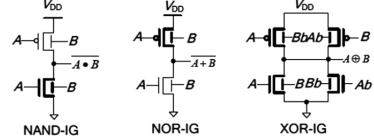(a) Complementary static logic gates using SG FinFETs




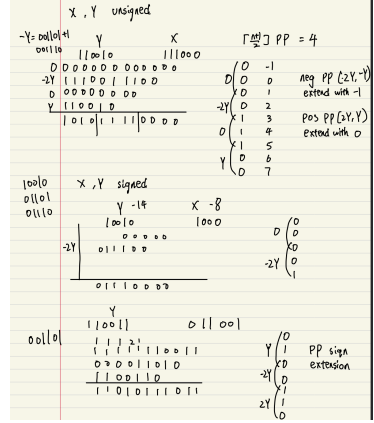(b) Compact complementary static logic gates using dual- V_{DD} IG FinFETs



Gate type	Logical effort	Formula	$n = 2$ $\gamma = 2$	$n = 3$ $\gamma = 2$	$n = 4$ $\gamma = 2$
NAND	total	$\frac{n(n+1)}{1+\gamma}$	8/3	5	8
	per input	$\frac{n+1}{1+\gamma}$	4/3	5/3	2
NOR	total	$\frac{n(1+\gamma)}{1+\gamma}$	10/3	7	12
	per input	$\frac{1+\gamma}{1+\gamma}$	5/3	7/3	3
multiplexer	total	$4n$	8	12	16
	d_{equiv}	2.2	2.2	2.2	2.2
XOR, XNOR, parity (symmetric)	total	$n^2 2^{n-1}$	8	36	128
	per bundle	$n 2^{n-1}$	4	12	32
XOR, XNOR, parity (asymmetric)	total		8	24	48
	per bundle		4.4	6.12, 6	8, 16, 16, 8
majority (symmetric)	total			12	4
	per input			4	
majority (asymmetric)	total			10	
	per input			4.4, 2	
C-element	total	n^2	4	9	16
	per input	n	2	3	4
latch (dynamic)	total	4			
	d_{equiv}	2.2			
upper bounds	total	$\frac{n^2 2^{n-1}}{1+\gamma}$	32/3	48	512/3
	per bundle	$\frac{n 2^{n-1}}{1+\gamma}$	16/3	16	128/3

Table 4.1: Summary of calculations of the logical effort of logic gates.

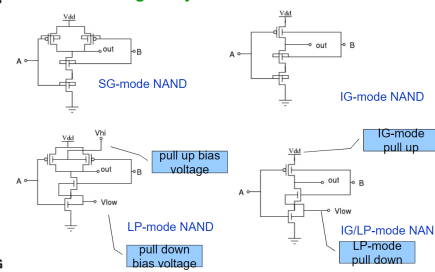

SG-mode NAND

IG-mode NAND

LP-mode NAND

IG/LP-mode NAND

pull up bias voltage

pull down bias voltage

pull up

pull down

Predecoders

1-of-4-Hot Predecoded Lines

word0

word1

word2

word3

word15

word0

word1

word2

word3

word15

word0

word1

word2

word3

word15

word0

word1

word2

word3

word15



word0

word1

word2

8-to-3 encoder [edit]

Truth Table								Output		
Input										
i ₇	i ₆	i ₅	i ₄	i ₃	i ₂	i ₁	i ₀	O ₂	O ₁	O ₀
0	0	0	0	0	0	0	0		x	
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

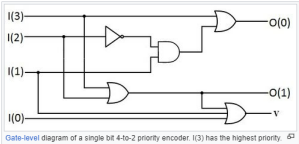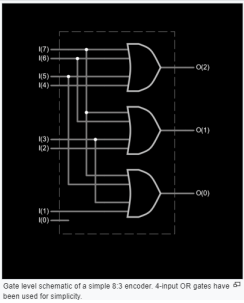

A truth table of a single bit 4-to-2 priority encoder is shown, where the inputs are shown in decreasing order of priority left-to-right, and "x" indicates a *don't care term* - i.e. any input value there yields the same output since it is superseded by a higher-priority input. The (usually-included) "v" output indicates if the input is valid.

4 to 2 Priority Encoder						
Input				Output		
i ₃	i ₂	i ₁	i ₀	O ₁	O ₀	v
0	0	0	0	x		0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1